

UNIT – IV

8. (a) What is full-subtractor ? Design a full-adder and implement the same using gates. 8
- (b) What is a BCD to seven-segment Decoder ? Design and implement it. 8
9. Explain the following :
- (a) Code Converters 8
- (b) Comparators 8

Roll No. ....

97664

BCA 1st Semester (New)  
Examination – November, 2017

LOGICAL ORGANIZATION OF COMPUTER - I

Paper : BCA-104

Time : Three Hours ] [ Maximum Marks : 80

*Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

Note : Question No. 1 is compulsory. Attempt four questions by selecting one question from each Unit. All questions carry equal marks.

1. (a) What is a multiplexer ? Outline its relevance.  $2 \times 8 = 16$
- (b) What is Unicode ? State its relevance.
- (c) What are Demultiplexers ? State their importance.
- (d) What are digital signals ? Explain.
- (e) What is the smallest and largest integer number represented in a 32-bit computer ?

(f) What are Venn Diagrams ?

(g) Prove  $x \cdot y' + y \cdot z' + z \cdot x' = x' \cdot y + y' \cdot z + z' \cdot x$ , algebraically.

(h) What are encoders ?

### UNIT - I

2. (a) Which number system is followed in digital computers and why ? 4

(b) Find out the values of X, Y and Z in the following :

$$(108.750)_{10} = (X)_2 = (Y)_8 = (Z)_{16} \quad 12$$

3. Explain the following :

(a) Error detection and correction codes 8

(b) Character Codes 8

### UNIT - II

4. (a) What are De-Morgan's Law ? Illustrate. 6

(b) Kush wants to purchase a bicycle. The bicycle must have brakes. He will buy a bicycle that has either a hand-brake or a foot-brake. No bicycle has both types. Write the Boolean equation for buying a bicycle. Implement the same using basic gates. 10

5. Explain the following :

(a) Duality principle 6

(b) Canonical forms of Boolean Functions 5

(c) Boolean Axioms 5

### UNIT - III

6. (a) What are Universal Gates ? Why these are named so ? Justify. 6

(b) What do you mean by multilevel NAND and NOR circuits ? Illustrate. 5

(c) What are AND-OR-INVERT and OR-AND-INVERT implementation ? Explain. 5

7. (a) What is combinational circuit ? What are its characteristics ? Detail out the procedure for design of combinational circuit. 8

(b) Design a combinational circuit that receives 2-bit binary input and produces its square at the output. 8