

Dec. 2005

**Section - A (Marks : 2 each)**

- Q. 1 (a) Write the first four decimal digits in base 4.  
(b) Convert the following logic function in a product of maxterms  
 $F(A, B, C) = (A' + B)(B' + C)$ .  
(c) Implement the Boolean function with three half-adder circuits  
 $F = A'BC + AB'C$ .  
(d) Define the terms decoder and demultiplexer.  
(e) Perform the subtraction with the following unsigned binary  
number by taking the 2's complement of the subtrahend  
11010-10000  
(f) Give the logic diagram and characteristic table of a clocked D  
Flip-flop.  
(g) What is the role of Binary Ripple Counter ?  
(h) Explain the role of PAL and PLA in digital design.  
(i) What is the difference between hardwired control and micro  
programmed control ?  
(j) What is the need of converting digital data into analog data ?

**Section - B (Marks : 5 each)**

- Q. 2 Write a short note on transmission line effects.  
Q. 3 Given an overview of Custom VLSI design.  
Q. 4 Design a 16-bit ring counter with 4-bit shift registers.  
Q. 5 Show the contents of an 8-bit register that stores the numbers +33  
and -33 in sign - 1's complements and sign 2's complement  
form.  
Q. 6 Write a short note on DTL Digital circuit technology.

**Section - C (Marks : 10 each)**

- Q. 7 Explain in detail the various types of memory systems used in  
digital design.

1. Discuss the advantage of a binary ladder network over a binary  
weighted register chain in D/A converter.  
2. Design and draw the circuit of a shift register to generate the  
following wave train ..... 1101011 .....  
3. Give the flowchart of PLD design, programming and test process.  
4. Design a combinational logic circuit for converting Gray code to  
binary.