

- (d) Describe the advantage of using PLA over ROM for realizing some Boolean functions.
- (e) What is the role of Binary Counter?
- (f) What is the difference between custom and semi-custom design in VLSI?
- (g) Why we need D/A techniques?
- (h) What do you mean by PLD's?

Section - B (Marks : 5 each)

- 1 Describe the advantage of using PLA over ROM for realizing some Boolean functions.
- 2 Write a short note on transmission line effects.
- 3 Show the contents of an 8-bit register that stores the numbers +33 and -33 in binary and sign 2's complement form.
- 4 Design a simple BCD-to-seven-segment decoder.
- 5 Write a short note on MOS Digital circuit technology.

Section - C (Marks : 10 each)

- 7 Explain in detail the various Bus structures used in digital design.
- 8 (a) Give the flow chart of PLD design, programming and test process.
(b) A computer employs RAM chips of 256×8 and ROM chips of 1024×8 . The computer system needs 2K bytes of RAM, 4 K bytes of ROM, and four interface units, each with four registers. A memory-mapped I/O configuration is used. The two highest order bits of the address bus are assigned 00 for RAM, and 10 for interface registers. How many ROM and RAM chips are needed?
- 9 (a) Explain how a shift register can be used to generate or check a parity.
(b) A certain 12 bit BCD D/A converter has a full-scale output of 9.99 V.
Determine the percent resolution.
Determine the converter's step size.

May 2005

Section - A (Marks : 2 each)

1. What is the difference between a product of maxterms and a sum of minterms?
2. Implement the Boolean expression $F(A, B, C) = A'B + A'B'C + ABC$ using three half-adder circuits.
3. What do you mean by BCD adder?
4. Perform the subtraction with the following unsigned binary number by taking the 2's complement of the subtrahend $1101 - 1000$.