

Roll No. ....

Total No. of Questions : 09]

[Total No. of Pages : 02

**B.Tech. (Sem. - 3<sup>rd</sup>)**

**DIGITAL CIRCUITS & LOGIC DESIGN**

**SUBJECT CODE : CS - 205**

**Paper ID : [A0453]**

[Note : Please fill subject code and paper ID on OMR]

**Time : 03 Hours**

**Maximum Marks : 60**

**Instruction to Candidates:**

- 1) Section - A is **Compulsory**.
- 2) Attempt any **Four** questions from Section - B.
- 3) Attempt any **Two** questions from Section - C.

**Section - A**

**Q1)**

**(10 x 2 = 20)**

- a) Solve  $(10101)_2 - (10011)_2$ .
- b) Subtract  $(11001)_2$  from  $(11101)_2$  using 2's complement method?
- c) State De-Morgans theorem?
- d) Name three types of TTL gates?
- e) What does the term driver mean in a decoder?
- f) List two applications of Multiplexer?
- g) Which flip flop is preferred for data transfer?
- h) What is a volatile memory?
- i) Which is the fastest ADC among available ADCs?
- j) What is a ring counter?

### Section - B


(4 x 5 = 20)

- Q2) What is a BCD code? What are its advantages and disadvantages?
- Q3) Prove that if  $A + B = A + C$  and  $A' + B = A' + C$ , then  $B = C$ .
- Q4) With the help of circuit diagram explain working of a two input TTL NAND gate?
- Q5) Describe with diagram internal architecture of PAL?
- Q6) Design a circuit that will generate an even parity bit for 4 bit input and implement it using only NAND gates?

### Section - C

(2 x 10 = 20)

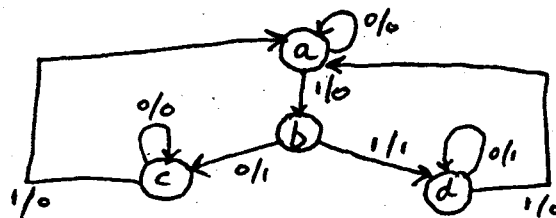- Q7) (a) Explain the difference in operation of a monostable and astable multivibrator?  
(b) What is master slave JK flip flop / Explain its working?
- Q8) Design a circuit that will function according to state diagram given below:



- Q9) (a) Implement the function  
 $F = A'BC + ABC' + A'B'C' + AC'$  using PAL.  
(b) With help of neat diagram explain working of R-2R ladder type DAC.

