

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages: 02
Total No. of Questions: 09

B. tech (Sem.-3rd)
DIGITAL CIRCUIT & LOGIC DESIGN
Subject Code: BTCS-303
Paper ID: [A1125]

Time: 3 Hrs.

Max. Marks: 60

INSTRUCTIONS TO CANDIDATE:

1. *Section-A is compulsory.*
2. *Attempt any 4 questions from Section-B. And any two questions from Section-C.*

SECTION-A

[Marks: 02 each]

- Q.1.** (a) State Duality Theorem.
(b) What is the difference between k- map and Qm method?
(c) Differentiate Combinational and Sequential Circuits.
(d) What do you mean by non-weighted code? Give example.
(e) What is Bidirectional shift register?
(f) How many flip flops are required for Mod- 6 Counter?
(g) Differentiate Static RAM and Dynamic RAM.
(h) What is the importance of parity bit?
(i) Differentiate Moore and Mealy Machines.
(j) Discuss the following:
a) Noise Margin b) Fan in

SECTION-B

[Marks: 05 each]

- Q.2.** What is a Decoder? Compare a decoder and a demultiplexer with suitable block diagrams.
Q.3. Explain the concept of Triggering? Also differentiate Edge Triggering and level Triggering.
Q.4. Draw and explain the operation of TTL NAND Gate.
Q.5. Design a full Subtractor circuit using NAND gates only.
Q.6. Draw the circuit diagram of a mod-10 Synchronous Counter.

SECTION-C

[Marks: 10 each]

- Q.7.** What is Race Around Condition? How it can be avoided. Also discuss the working of Master Slave J-K Flip Flop.
- Q.8.** Write a note on following:-
- (a) Boolean Algebra
 - (b) Magnitude Comparator
 - (b) ASCII Code
 - (d) Multiplexer Tree
- Q.9.** Draw the circuit of a R-2R ladder D-A converter and explain its operation. Also determine the resolution of the output from a DAC that has a 12-bit input.

....END.....