

Total No. of Questions : 09]

[Total No. of Pages : 02

**B.Tech. (Sem. - 3<sup>rd</sup>)**  
**DIGITAL CIRCUITS AND LOGIC DESIGN**  
**SUBJECT CODE : CS - 205**  
**Paper ID : [A0453]**

[Note : Please fill subject code and paper ID on OMR]

**Time : 03 Hours**

**Maximum Marks : 60**

**Instruction to Candidates:**

- 1) Section - A is **Compulsory**.
- 2) Attempt any **Four** questions from Section - B.
- 3) Attempt any **Two** questions from Section - C.

**Section - A**

**Q1)**

**(10 × 2 = 20)**

- a) Convert binary number 1001 into gray.
- b) Find SOP form of  $f = AB + BC + \bar{A}$ .
- c) Implement half subtractor using NAND gates.
- d) Find % age resolution of a 12 bit BCD input D/A converter which has full scale o/p of 29.97 V.
- e) Convert a D flip flop into a T flip flop.
- f) Differentiate between Asynchronous counter and Synchronous counter.
- g) What is significance of figure of merit of flip flops.
- h) Design a 4 : 1 mux.
- i) Classify logic families on the basis of number of gates on a single chip.
- j) Write pros and cons of SRAM and DRAM cell.

**Section - B**

**(4 × 5 = 20)**

**Q2)** Design a combinational ckt with 3 inputs and 1 output. The output is high only when more than one input is high.

**Q3)** Design a MOD 6 counter using T-flip flops.

**R-742**

**P.T.O.**

**Q4)** What are multivibrator circuits. Explain Astable multivibrator with the help of circuit diagram.

**Q5)** Explain the operation of two input TTL NAND gate.

**Q6)** Using Boolean Algebra show that

$$(A + B)(\bar{A} + C)(B + C) = AC + B\bar{A}$$

### Section - C

(2 × 10 = 20)

**Q7)** Design a comparator circuit which compares two 2 bit numbers. It has three outputs  $A > B$ ,  $A < B$  and  $A = B$ . Also show that  $A < B = \overline{A > B} \cdot \overline{A = B}$ .

**Q8)** Design a three bit, MOD 6, unit distance up-down counter.

**Q9)** What are programmable logic devices. What are their advantages. Explain in detail the architecture of a programmable logic device.

\* \* \*