

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(CSE/IT) (Sem.-3rd)

DIGITAL CIRCUITS AND LOGIC DESIGN

Subject Code : BTCS-303 (2011 Batch)

Paper ID : [A1125]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students has to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students has to attempt any TWO questions.

SECTION-A

1. Write briefly :

- a) State DeMorgan's theorems.
- b) What is a Multiplexer Tree?
- c) Differentiate Combinational and Sequential Circuits.
- d) What do you mean by weighted code? Give example.
- e) What is universal shift register?
- f) How many flip flops are required for Mod-6 Counter?
- g) Differentiate Static RAM and Dynamic RAM.
- h) What is the importance of parity bit ?
- i) Determine the resolution of the output from a DAC that has a 12-bit input.
- j) Differentiate Moore and Mealy Machines.

SECTION-B

2. What is a Decoder? Compare a decoder and a demultiplexer with suitable block diagrams.
3. Draw the circuit of a counter type A-D converter and explain its operation.
4. Design a full adder circuit using NAND gates only.
5. Draw the circuit diagram of a mod-5 synchronous counter.
6. Simplify the following expression using K-Map :

$$f(A,B,C,D) = \Sigma m(0, 3, 4, 5, 7, 8, 9) + d(10, 11, 12, 13, 14, 15) .$$

SECTION-C

7. What is Race around Condition? How it can be avoided? Also Discuss the working of Master Slave J-K Flip Flop.
8. Discuss the comparison of the important features of various IC logic families. Also draw and explain the operation of TTL NAND Gate.
9. Write a note on following :
 - a) Canonical POS
 - b) Boolean algebra.
 - c) Magnitude Comparator
 - d) Excess-3 Code.