

Roll No::.....

Total No. of Questions: 09

MAY-2014

[Total No. of Pages: 01]

B. Tech. CSE(Sem. – 3rd)
DIGITAL CIRCUITS & LOGIC DESIGN (BTCS - 303)

Time: 03 Hours

Maximum Marks : 60

Instruction to Candidates:

- 1) Section - A is **Compulsory**.
- 2) Attempt any **Four** questions from Section - B.
- 3) Attempt any **Two** questions from Section - C.

Section – A

Q1)

(10x2=20)

- a). Find the signed 8-bit binary number equivalent to 7_{10} .
- b). How many AND gates are required to realize $Y = ACD + EF + GH$
- c). What is the difference between synchronous and asynchronous?
- d). What do you understand by nonvolatile memory?
- e). What is the use of EEPROM?
- f). Write the name of various types of Digital to Analog Convertors.
- g). What is the difference between edge triggering and level triggering?
- h). What is the use of static RAM?
- i). Define racing problem in JK-Flip flop.
- j). Write one advantage of CMOS logic family.

Section – B

(4x5=20)

Q2) State and prove De-Morgan's theorems.

Q3) Draw and explain the operation of TTL inverter.

Q4) Implement the function $f(w, x, y, z) = m(0, 1, 5, 7, 8, 10, 13, 14, 15)$ using two 8-way multiplexers with an active low enable, plus an OR gate.

Q5) Explain the working of ladder type Digital to Analog Convertor.

Q6) Write a short note on Field Programmable Gate Array.

Section – C

(2x10=20)

Q7) Find the minimum sum of products expression for the function

$f(a, b, c, d) = \sum m(1, 3, 4, 6, 7, 9, 11, 12, 13, 15)$ using QM method.

Q8) Design a MOD - 10 synchronous counter using J-K Flip-Flops. Explain its working with the help of timing diagram.

Q9) Discuss various types of Read only Memories in detail.

—————End—————