

**Total No. of Questions: 09**

**B.Tech. (CSE)/(IT) (2011 Onwards) (Sem. – 3)**

**DIGITAL CIRCUITS & LOGIC DESIGN**

**M Code: 56593**

**Subject Code: BTCS-303**

**Paper ID: [A1125]**

**Time: 3 Hrs.**

**Max. Marks: 60**

**INSTRUCTIONS TO CANDIDATES:**

1. **SECTION-A** is **COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

**SECTION A**

1. Write briefly:

- a) Weighted BCD
- b) Principle of Duality
- c) Exclusive-NOR versus Exclusive-OR
- d) Multiplexer versus Demultiplexer
- e) Uses of Shift Registers
- f) FPGA
- g) Convert  $10101_2$  to decimal
- h) TTL and CMOS
- i) Number of Gate inputs required for expression:  $ABC + \bar{A}\bar{B}CD + \bar{E}\bar{F} + AD$
- j) MOSFET

### SECTION B

2. Evaluate Following:
  - a) Multiply  $2A8_{16}$  by  $B6_{16}$
  - b) Subtract 14 from 46 using 8-bit 2's complement arithmetic.
3. State and prove De-Morgan's Theorems.
4. Explain the Operation of two input TTL NAND gate.
5. Design and implement a 4-bit binary to gray convertor.
6. Distinguish between combinational and sequential switching circuits.

### SECTION C

7. Write short note on following
  - a) Successive approximation A to D conversion technique
  - b) Ripple Carry Adder
8. What are programmable logic devices? What are their advantages? Explain in detail the architecture of a programmable logic device.
9. Using Boolean algebra show that
  - a)  $AB + \bar{A}C + BC = AB + \bar{A}C$
  - b)  $AB + \bar{A}C = (A+C)(\bar{A} + B)$