

SECTION B

2. Reduce the following expression using K-map method and specify the Selective Prime Implicant (SPI), Redundant Prime Implicant (RPI), and Essential Prime Implicant (EPI).
$$F(A, B, C, D) = \sum m(1, 5, 6, 7, 11, 12, 13, 15)$$
3. What is excitation table? Design JK flip flop from SR flip flop by the use of excitation table.
4. Convert following number system
 - a) $(12.25)_{10} = (?)_2$
 - b) $(10101.1101)_2 = (?)_{16}$
 - c) $(125)_8 = (?)_{10}$
 - d) $(34)_{16} = (?)_2$
 - e) $(67.2)_8 = (?)_2$
5. Design 3-bit synchronous counter using JK flip flop. Also draw the counting sequence for the same.
6. What is the application of digital to analog converter? Explain R/2R ladder digital to Analog Converter with neat diagram.

SECTION C

7. What is programmable logic array? Implement programmable logic array (PLA) for given functions:

$$F1 = AB' + AC + A'BC'$$

$$F2 = AC + BC$$

8.
 - a) Design a 3 bit Gray to Binary code converter.
 - b) Design a 3 bit even parity generator and show its truth table.
9.
 - a) Distinguish between a half adder and a full adder with the help of truth table and logic diagram.
 - b) With the help of logic diagram and truth table, explain an octal to binary encoder.