

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(CSE / IT) (Sem.-3)
DIGITAL CIRCUITS AND LOGIC DESIGN

Subject Code : CS-205

Paper ID : [A0453]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A

Q1) Write briefly :




- a) Differentiate between synchronous and asynchronous counters.
- b) How do Demultiplexer differ from Decoder?
- c) Subtract -26 from 67 using 2's complement.
- d) Are CMOS memory chips better over bipolar memory chips? Comment.
- e) Convert : $(153.513)_{10} = ()_8$
- f) Outline two major applications of multi-vibrators?
- g) What is meant by resolution of an A/D convertor?
- h) Find x : $(BEE)_x = (2699)_{10}$
- i) A preset able counter has sixteen flip-flops. If the preset number is 125, what is the modulus?
- j) What is the minimum voltage value that is considered as high stage input for TTL logic family?

SECTION-B

- Q2) Draw the logic symbol and construct the truth table for each of the following gates :
- Three input NAND gate
 - Two input OR gate
 - Three input EX-NOR gate
- Q3) What is an Encoder? Compare a decoder and a Multiplexer with suitable block diagrams.
- Q4) Design a MOD-3 synchronous counter using J-K Flip Flops.
- Q5) Differentiate between static MOS and Dynamic MOS RAM. Explain the working of a static MOS RAM cell with the help of a circuit diagram.
- Q6) State and prove De-Morgan's Theorem for three variables.

SECTION-C

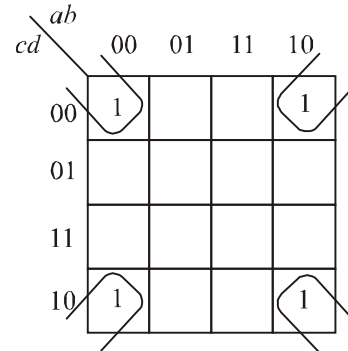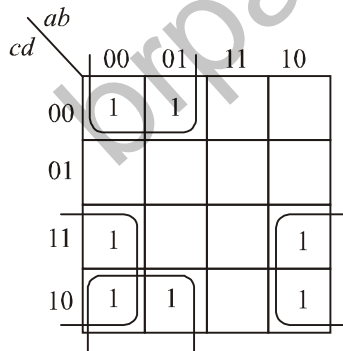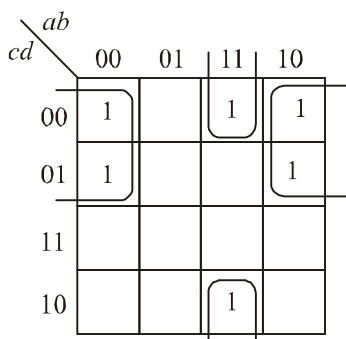- Q7) Write out the minimized Boolean Algebra Expression for each of the Karnaugh maps below. Also, Construct Truth tables for each of the maps.



- Q8) Elaborate VLSI design with an example of custom and semi-custom design.
- Q9) Write short notes on :
- Semiconductor memories
 - Bus Structures